



# SHIFT REGISTERS

# INTRODUCTION

- A sequential logic circuit, mainly for storage of digital data and movement
- A group of flip-flops connected in a chain so that the output from one flip-flop becomes the input of the next flip-flop.
- All the flip-flops are driven by a common clock, and all are set or reset simultaneously.
- Types:
  - Serial In – Serial Out,
  - Serial In – Parallel Out,
  - Parallel In – Serial Out,
  - Parallel In – Parallel Out, and
  - Bidirectional shift registers.
  - A special form of counter – the shift register counter, (Ring and Johnson)


Remember: A flip-flop stores one bit of information

When you want to store  $n$  bits → register,


- ‘ $n$ ’ flip-flops used,
- Clock is shared by all so action is synchronous with clock edge
 
# REVIEW: THE D FLIP-FLOP

- D flip flop is used to store binary Data.
- The logic level at the “D” (data) input is transferred to the Q output when the clock is asserted.
- It remains stored at output Q until the clock is asserted a second time.



 
- If look inside the D flip flop, you can see how it works.



- Let's assume the initial conditions at Q are 0.
- Set D to logic 1.
- Show the logic levels at S and R
- The internal SR inputs are in the set mode. The flip flop will set if D=1 and the clock is asserted.  $Q = D$ !
- Set D to logic 0.
- The internal SR inputs are in the reset mode. The flip flop will reset if D=0 and the clock is asserted.  $Q = D$  again!
 
# 4-BIT SHIFT REGISTER

- The **4-bit shift register** can shift data from QA to QB to QC to QD. The shift register will be filled with 1's then it will be filled with 0's.
- Assume the initial conditions are :  $Qa=Qb=Qc=Qd=0$ .
- Din is the input to QA. The data at QA shifts to QB. The data at QB shifts to QC. QC shifts to QD.
- Apply a logic 1 at input Din and clock the shift register 4 times.
- You have seen how it takes 4 clock pulses to fill the shift register with 1's. Din will now be connected to logic 0. This will shift the 1's out and fill the shift register with 0's.



# FUNCTIONS OF SHIFT REGISTER

## ➤ **Storage Capacity**

- ✓ Total no. of bits of digital binary word (data) that can be stored
- ✓ Each flip-flop in shift register stores 1 bit
- ✓ The no. of flip-flop in shift register determines storage capacity


## ➤ **Shifting Capability**

- ✓ Movement of data from stage to stage within register or into or out of register upon the application of clock pulse
- ✓ Shifting can be done either in right direction or left direction


# OPERATIONS ON SHIFT REGISTER

- Parallel and Serial Data Transmission
  - ✓ Shift registers are often used to interface digital systems situated remotely from each other.
  - ✓ Task: We want to transmit an  $n$ -bit quantity between two location that are far from each other.
- Options:
  - ✓ Use  $n$  lines to transmit  $n$  bits in parallel. Problem: Cost is expensive.
  - ✓ Use a single line to transmit the information serially, one bit at a time. Cost is less.

 
# OPERATIONS ON SHIFT REGISTER (LOADING, SHIFTING, ROTATING)




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in/parallel out

 

(f) Rotate right

 


(g) Rotate left


 
# SERIAL IN SERIAL OUT (SISO)

- Data entered into a register serially one bit at a time
- Output is also obtained in serial form
- On the leading edge of the first clock pulse, the signal on the INPUT (data\_input) is latched in the first flip-flop.
- On the leading edge of the next clock pulse, the contents of the first flip-flop is stored in the second flip-flop, and the signal which is present at the INPUT (data\_input) is stored in the first flip-flop, etc.
- A 3-bit SISO shift register can be constructed using 3-D flip-flops
- Clock is provided in synchronous way in positive edge




WRITE	FF0	FF1	FF2	FF3
1001	0	0	0	0



 
# FOR DATA INPUT 011

- The register is first cleared, forcing all three outputs to zero.
- The input data is then applied sequentially to the D input of the first flip-flop on the left (FF0).
- During each clock pulse, one bit is transmitted from left to right.
- The least significant bit of the data has to be shifted through the register from FF0 to FF2.




# TIMING DIAGRAM (SISO)

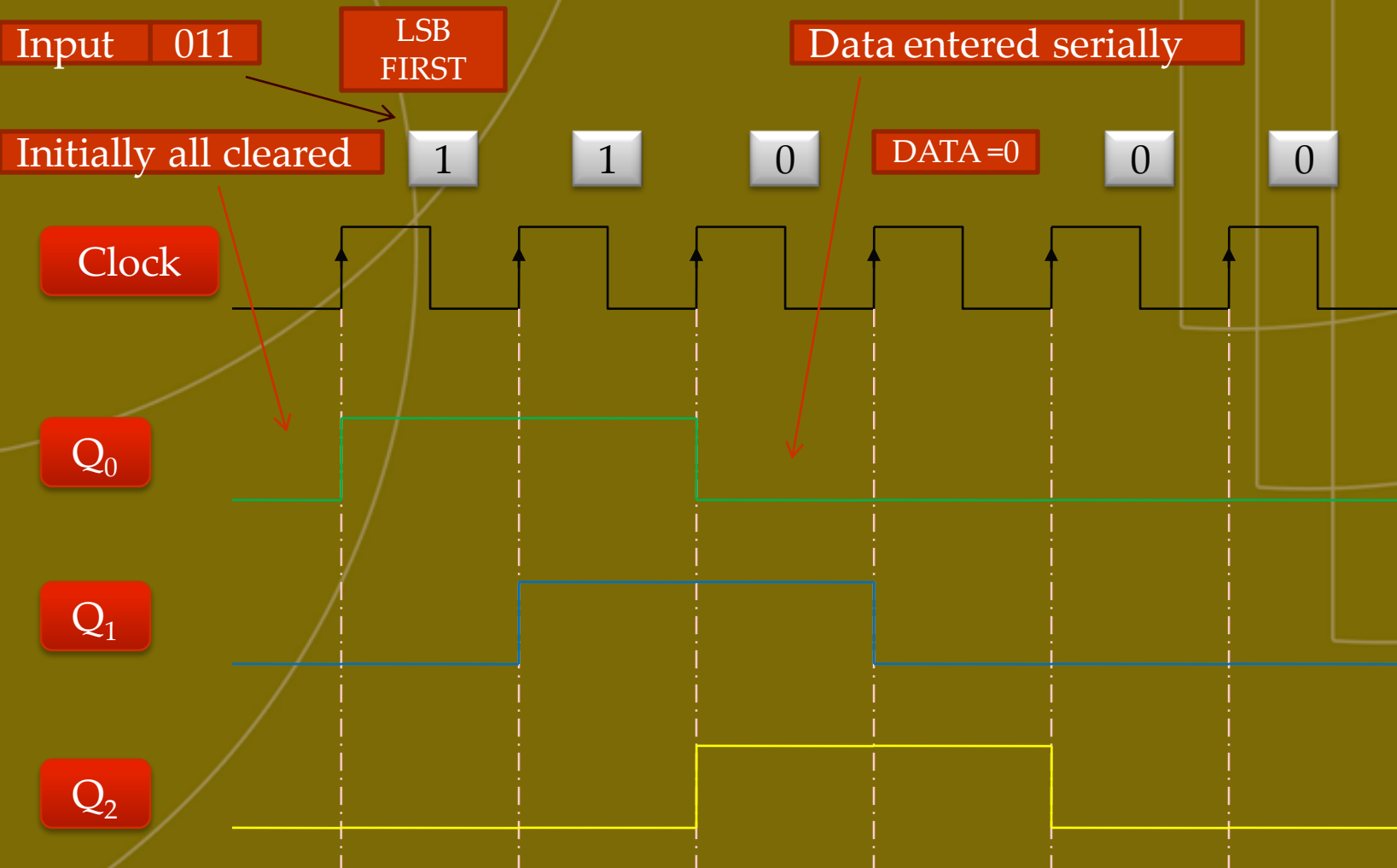
 
# SERIAL IN PARALLEL OUT (SIPO)

- Data entered into a register serially one bit at a time
- Output is obtained in parallel form
- On the leading edge of the first clock pulse, the signal on the INPUT is latched in the first flip-flop.
- On the leading edge of next clock pulse, the content of first flip-flop is stored in the second flip-flop, and the signal, present at the INPUT is stored in the first flip-flop, etc. as explained in previous section.
- **The difference is the way in which the data bits are taken out of the register.**
- Once the data are stored, each bit appears on its respective output line, and all bits are available simultaneously.
- A 3-bit SIPO shift register can be constructed using 3-D flip-flops
- Clock is provided in synchronous way in positive edge




CLEAR

1001


Q0	Q1	Q2	Q3
0	0	0	0
 
# FOR DATA INPUT 011

- The register is first cleared, forcing all three outputs to zero.
- The input data is then applied sequentially to the D input of the first flip-flop on the left (FF0).
- During each clock pulse, one bit is transmitted from left to right.
- The least significant bit of the data has to be shifted through the register from FF0 to FF2.




# TIMING DIAGRAM (SIPO)

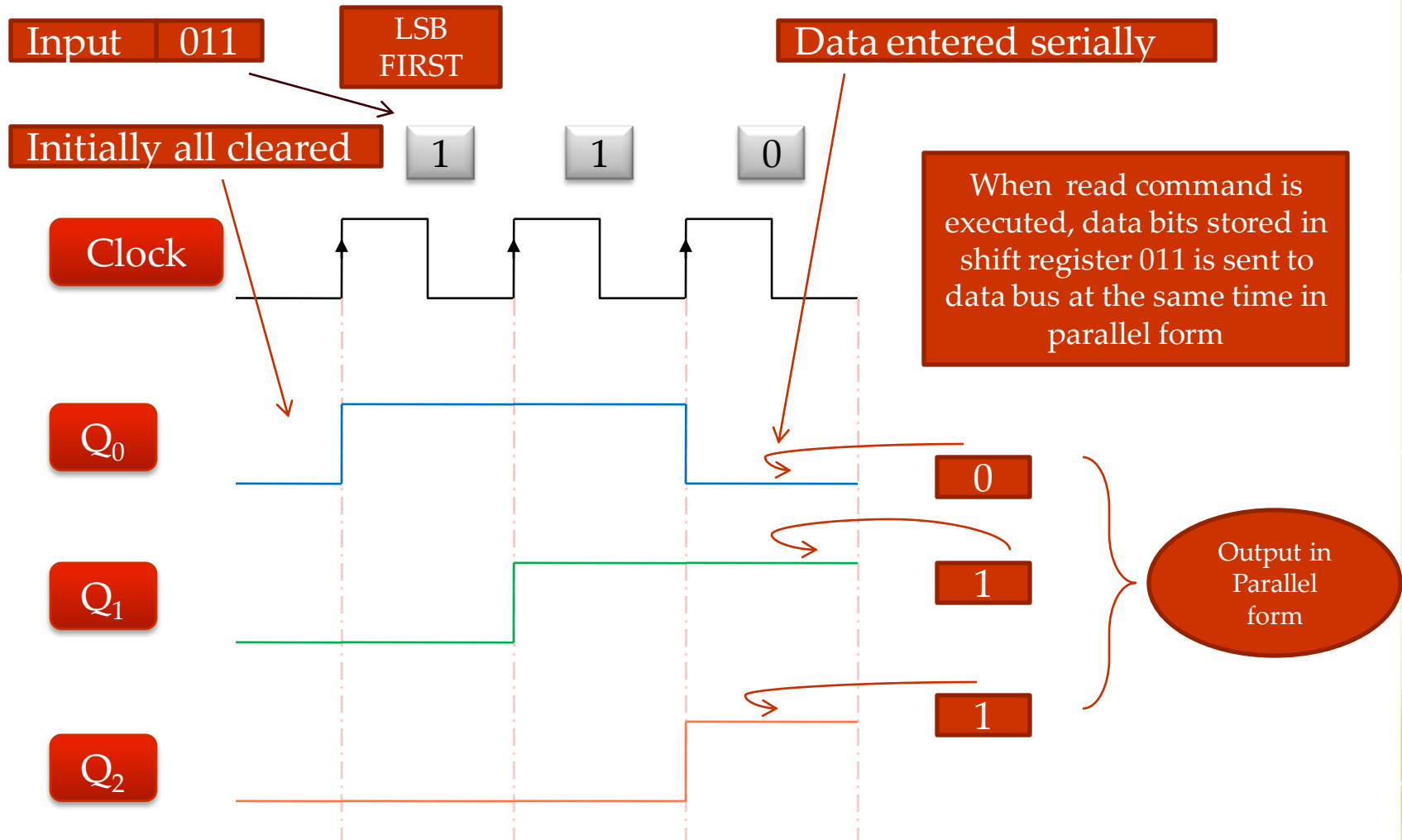

 
# PARALLEL IN PARALLEL OUT (PIPO)

- Data entered into a register simultaneously (all bits at the same time)
- Output is also obtained in parallel form
- Once the register is clocked, all data bits appear on the parallel outputs immediately following the simultaneous entry of the data bits at the D inputs.
- A 3-bit PIPO shift register can be constructed using 3-D flip-flops
- Clock is provided in synchronous way in positive edge
- The D's are the parallel inputs and the Q's are the parallel outputs.



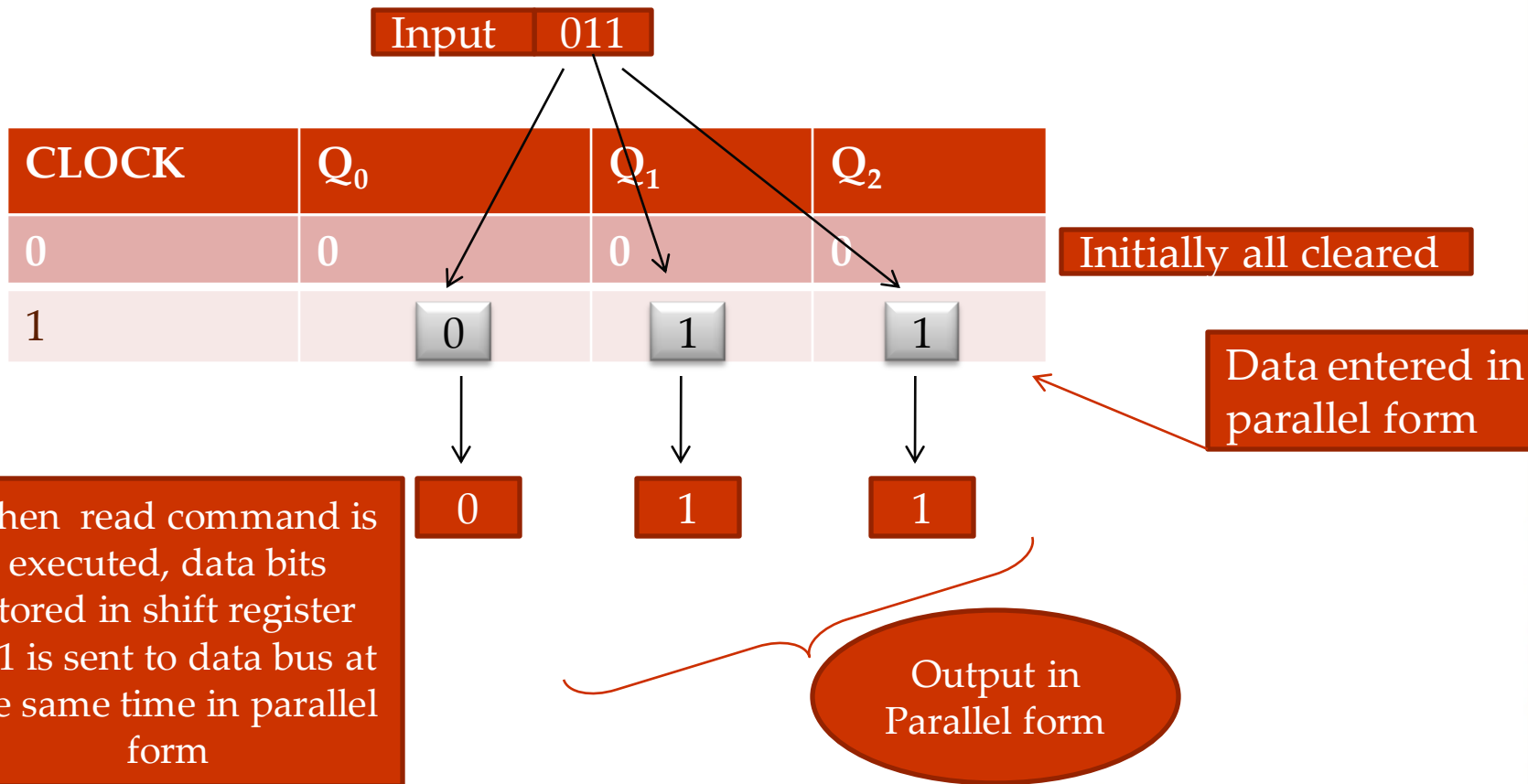
# FOR DATA INPUT 011

- The register is first cleared, forcing all three outputs to zero.
- Once the register is clocked, all the data at the D inputs (011) appear at the corresponding Q outputs simultaneously






# TIMING DIAGRAM (PIPO)

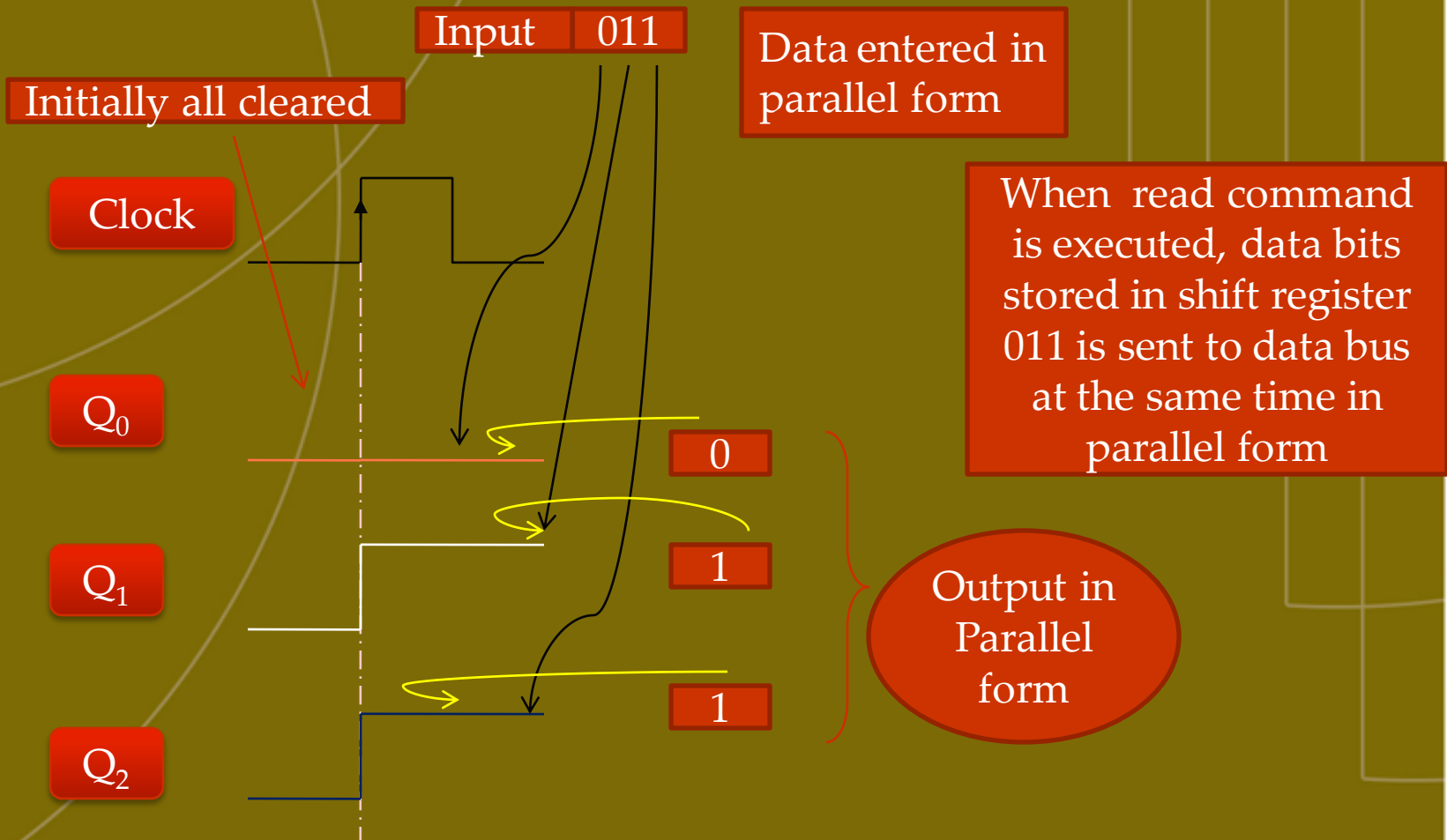


# PARALLEL IN SERIAL OUT (PISO)

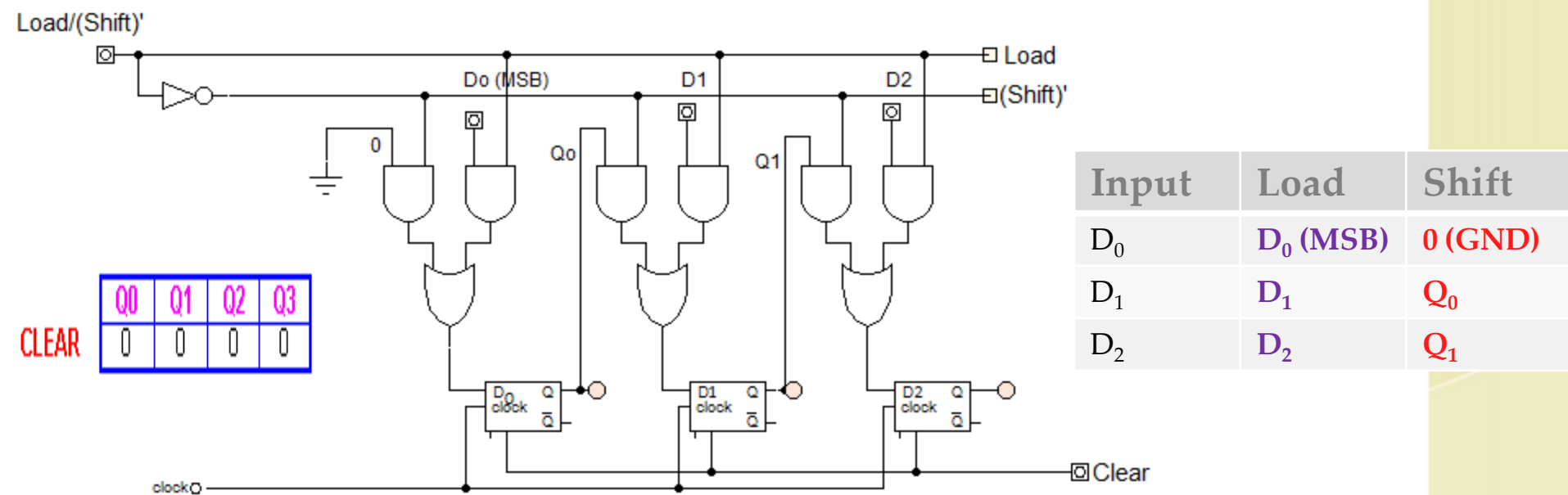


- Data entered into a register simultaneously (all bits at the same time)
- Output is also obtained in serial form
- A 3-bit PISO shift register can be constructed using 3-D flip-flops
- Clock is provided in synchronous way in positive edge
- D0, D1, D2 are the parallel inputs, where D0 is the most significant bit and D2 is the least significant bit.
- To write data in, the mode control line (Load/Shift) is taken to **HIGH** and the data is clocked in.
- The data can be shifted when the mode control line (Load/Shift) is **LOW** as SHIFT is active low. The register performs right shift operation on the application of a clock pulse.
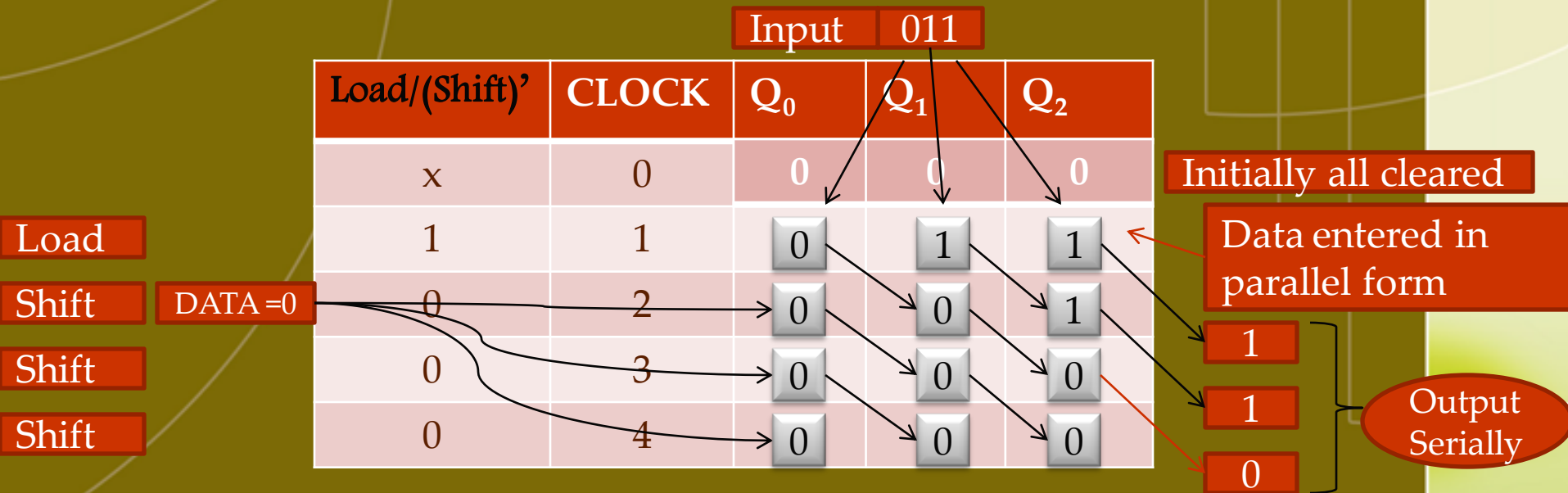
# FOR DATA INPUT 011


- The register is first cleared, forcing all three outputs to zero.
- To write data in, the mode control line (Load/(Shift)') is taken to **HIGH** and the data is clocked in.
- Once the register is clocked, all the data at the D inputs (011) appear at the corresponding Q outputs simultaneously.
- To read data out, the mode control line (Load/(Shift)') is **LOW** as SHIFT is active low.
- The register performs right shift operation on the application of a clock pulse.
- During each clock pulse, one bit is transmitted from left to right.



# TIMING DIAGRAM (PISO)

 

# BIDIRECTIONAL SHIFT REGISTER

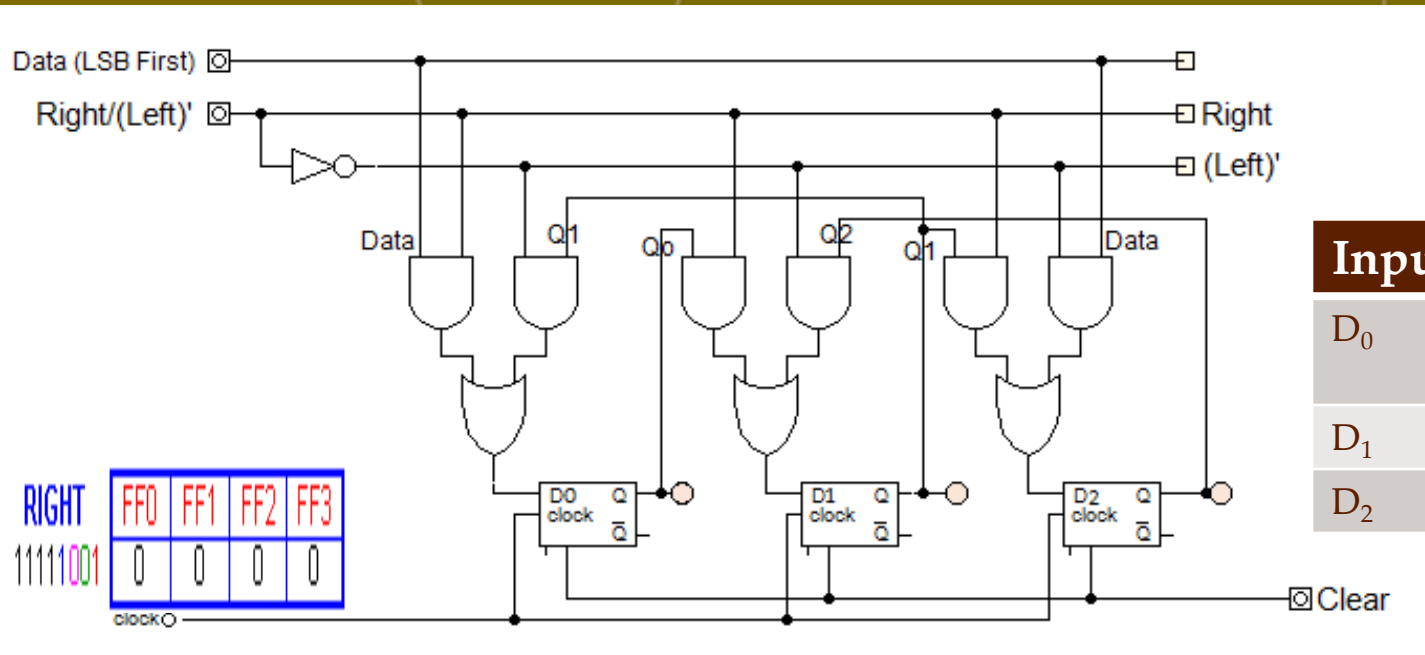


Input	Right	Left
D <sub>0</sub>	DATA (LSB FIRST)	Q <sub>1</sub>
D <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>
D <sub>2</sub>	Q <sub>1</sub>	DATA


- A Bidirectional, or reversible, shift register is one in which the data can be shift either left or right
- Data entered into and taken out of a register serially one bit at a time.
- A 3-bit Bidirectional shift register can be constructed using 3-D flip-flops
- Clock is provided in synchronous way in positive edge
- To shift right, the mode control line (Right/(Left)') is taken to **HIGH** and the data is clocked in.
- To shift left, the mode control line (Right/(Left)') is **LOW** as LEFT is active low. The register performs left shift operation on the application of a clock pulse.
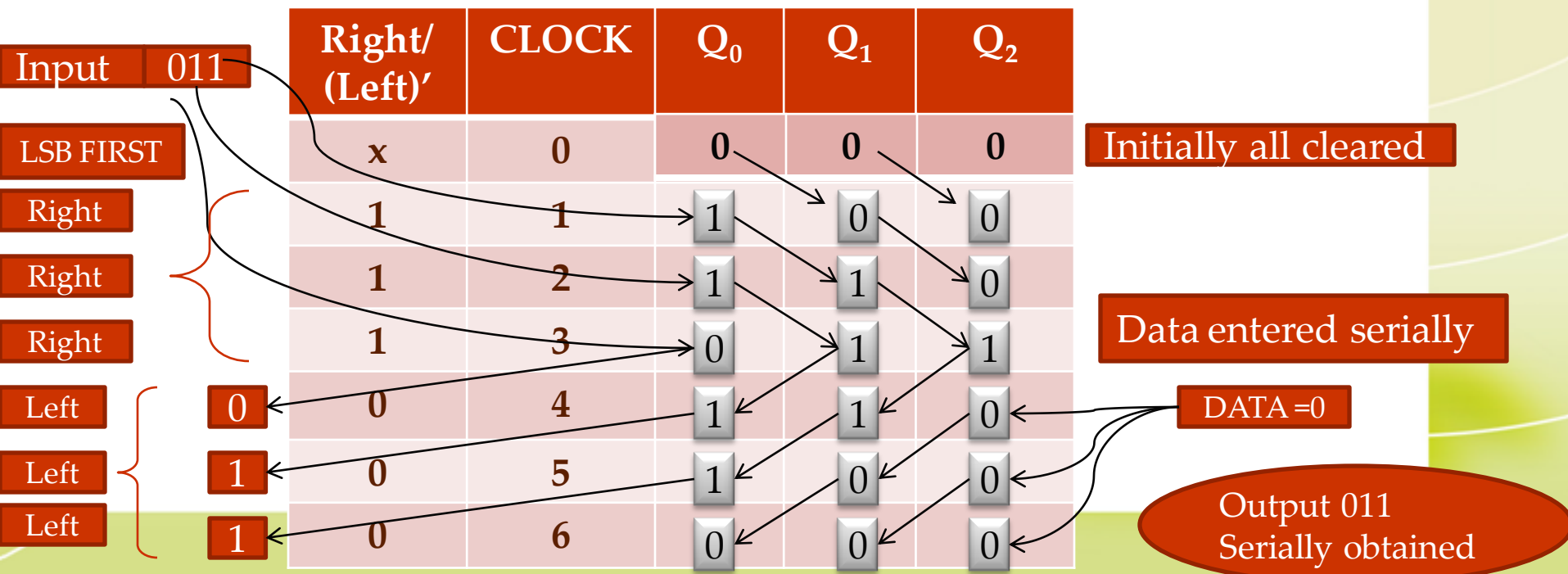
# FOR DATA INPUT 011

- The register is first cleared, forcing all three outputs to zero.
- To shift right, the mode control line (Right/(Left)') is taken to **HIGH** and the data is clocked in.
- During each clock pulse, one bit is transmitted from left to right serially.
- The least significant bit of the data has to be shifted through the register from First flip-flop to Last.
- To shift left, the mode control line (Right/(Left)') is **LOW** as LEFT is active low.
- The register performs left shift operation on the application of a clock pulse.
- During each clock pulse, one bit is transmitted from right to left serially



# TIMING DIAGRAM (BIDIRECTIONAL)

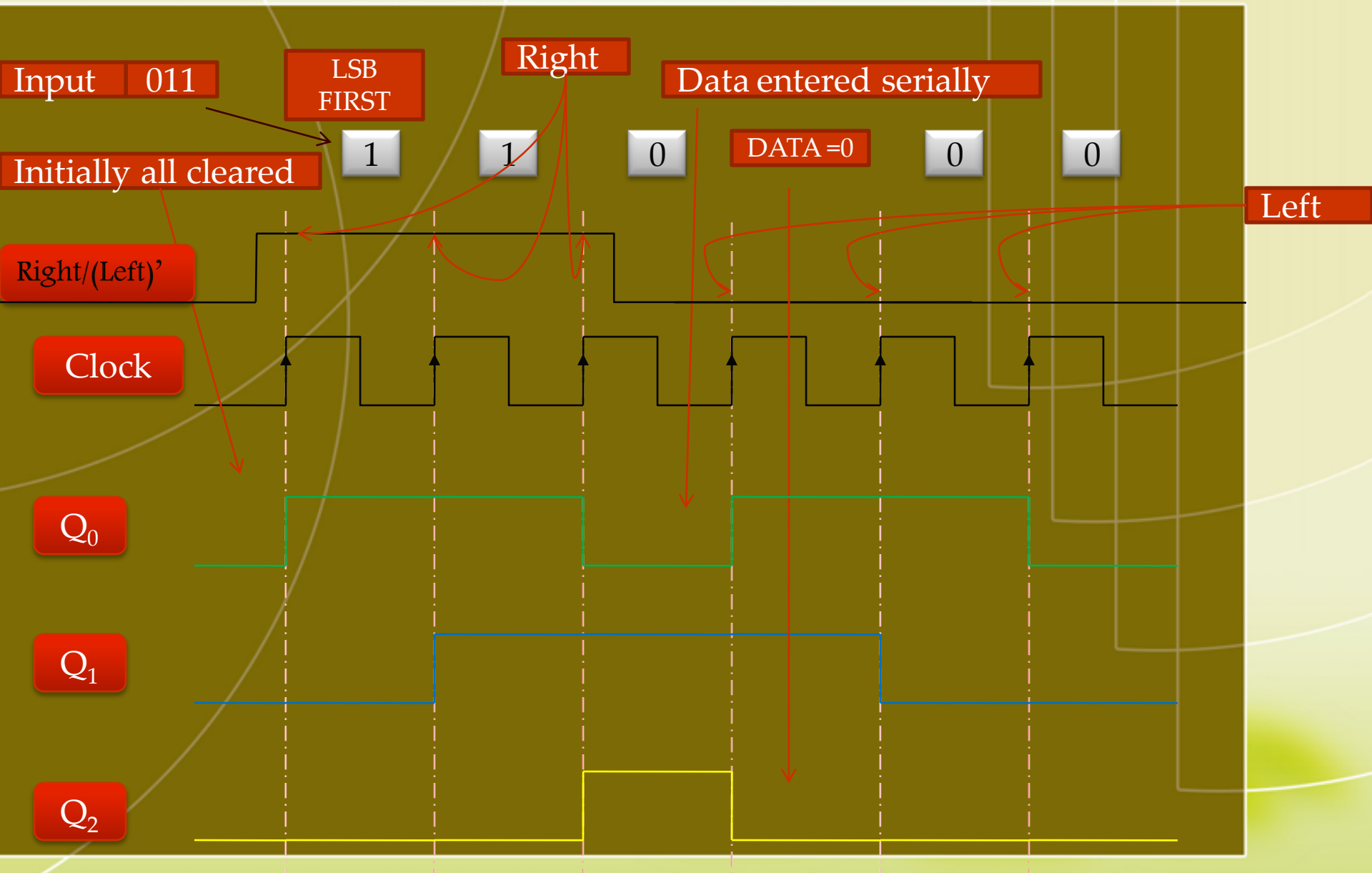




# SHIFT REGISTER COUNTERS

- Two of the most common types of shift register counters are
  - Ring counter and
  - Johnson counter.
- They are basically shift registers with the serial outputs connected back to the serial inputs in order to produce particular sequences.
- These registers are classified as counters because they exhibit a specified sequence of states.


# RING COUNTER

- Basically a circulating shift register (data moved in a ring)
- The output of the most significant stage (Last FF) is fed back to the input of the least significant stage (1<sup>st</sup> FF).
- Initially before clock pulse, , all the flip-flops except the first one FF0 are reset to 0 using clear and 1<sup>st</sup> FF (FF0) is preset to 1 instead.
- 4-bit Ring counter constructed from 4 D flip-flops.
- Clock is provided in synchronous way in positive edge
- The output of each stage is shifted into the next stage on the positive edge of a clock pulse serially.
- REMEMBER: N-Bit Ring Counter-----N Flip-Flops-----N states
- Since the count sequence has 4 distinct states, the counter can be considered as a mod-4 counter.
- Only 4 of the maximum 16 states are used, making ring counters very inefficient in terms of state usage.
- But the major advantage of a ring counter over a binary counter is that it is self-decoding. No extra decoding circuit is needed to determine what state the counter is in.


CLEAR	FF0	FF1	FF2	FF3
	1	0	0	0

 

# RING COUNTER

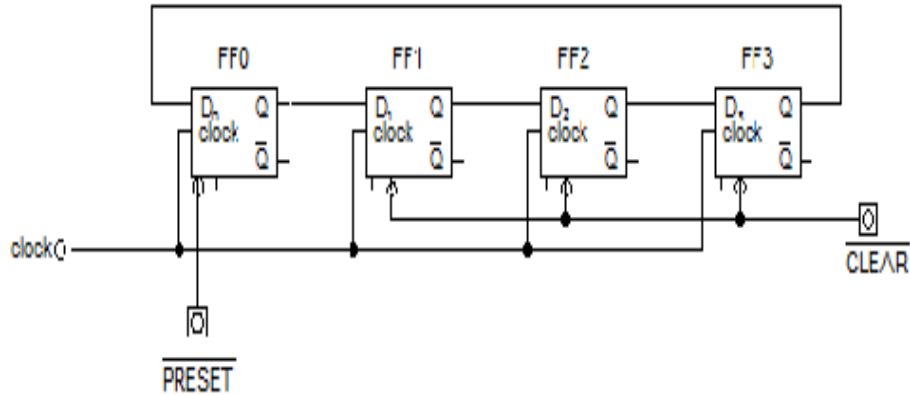

Clk	$Q_0$	$Q_1$	$Q_2$	$Q_3$
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1

 


# JOHNSON COUNTER


CLEAR

FF0	FF1	FF2	FF3
0	0	0	0


- a circulating shift register (data moved in a ring)
- A variation of standard ring counters, with the inverted output of the last stage fed back to the input of the first stage.
- They are also known as twisted ring counters.
- An  $n$ -stage Johnson counter yields a count sequence of length  $2n$ , so it may be considered to be a  $\text{mod-}2n$  counter
- Disadvantage is that the maximum available states are not fully utilized. Only eight of the sixteen states are being used for 4 bit Johnson counter
- Both Ring and Johnson counter must initially be forced into a valid state in the count sequence because they operate on a subset of the available number of states. Otherwise, the ideal sequence will not be followed
- Initially before clock pulse, , all the flip-flops are reset to 0 using clear
- 4-bit Johnson counter constructed from 4 D flip-flops.
- Clock is provided in synchronous way in positive edge
- The output of each stage is shifted into the next stage on the positive edge of a clock pulse serially.
- REMEMBER:  $N$ -Bit Johnson Counter----- $N$  Flip-Flops----- $2N$  states

 

# JOHNSON COUNTER

 

Clk	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

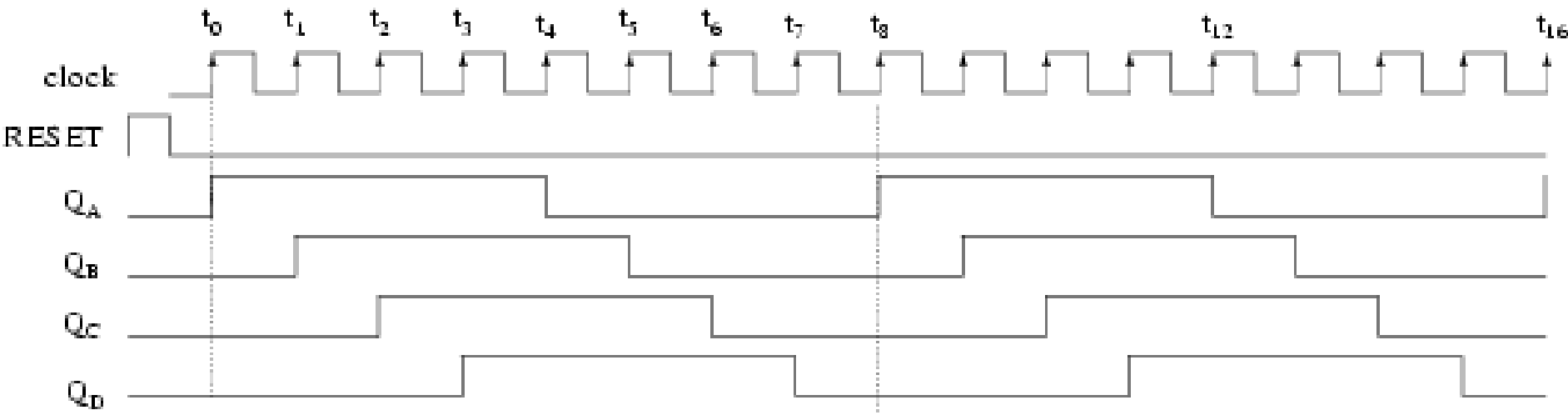

Four stage Johnson counter waveforms

# APPLICATION OF SHIFT REGISTERS

- To produce Time Delay
  - ✓ The serial in –serial out shift register can be used as a time delay device. The amount of delay can be controlled by
    - ✓ the number of stages in the register
    - ✓ the clock frequency
- To simplify combinational logic
  - ✓ The ring counter technique can be effectively utilized to implement synchronous sequential circuits.
  - ✓ A major problem in the realization of sequential circuits is the assignment of binary codes to the internal states of the circuit in order to reduce the complexity of circuits required.
  - ✓ By assigning one flip-flop to one internal state, it is possible to simplify the combinational logic required to realize the complete sequential circuit.
  - ✓ When the circuit is in a particular state, the flip-flop corresponding to that state is set to HIGH and all other flip-flops remain LOW.

# APPLICATION OF SHIFT REGISTERS

- **To convert serial data to parallel data**
  - ✓ A computer or microprocessor-based system commonly requires incoming data to be in parallel format.
  - ✓ But frequently, these systems must communicate with external devices that send or receive serial data.
  - ✓ So, serial-to-parallel conversion is required. As shown in the previous sections, a serial in – parallel out register can achieve this.

- **Parallel to Serial data converter** (PISO register can do this)

- **Multiplication of binary number by two.**

- ✓ Shift data one bit left to achieve this

Multiplication by 2					
4 bit SISO	0	1	1	0	=6
Left shift with 0	1	1	0	0	=12

- **Division of binary number by two.**

- ✓ Shift data one bit right is equivalent to dividing by 2 with an error of  $\frac{1}{2}$  in decimal value

Divisible by 2					
4 bit SISO	0	1	1	0	=6
Right shift with 0	0	0	1	1	=3



# APPLICATION OF SHIFT REGISTERS

- Data storage (PIPO)
- ✓ The common clock input triggers all flip-flops on the positive edge of each pulse → the binary data available at the 4 inputs are transferred into the register.
- ✓ The four outputs can be sampled to obtain the binary information stored in the register.

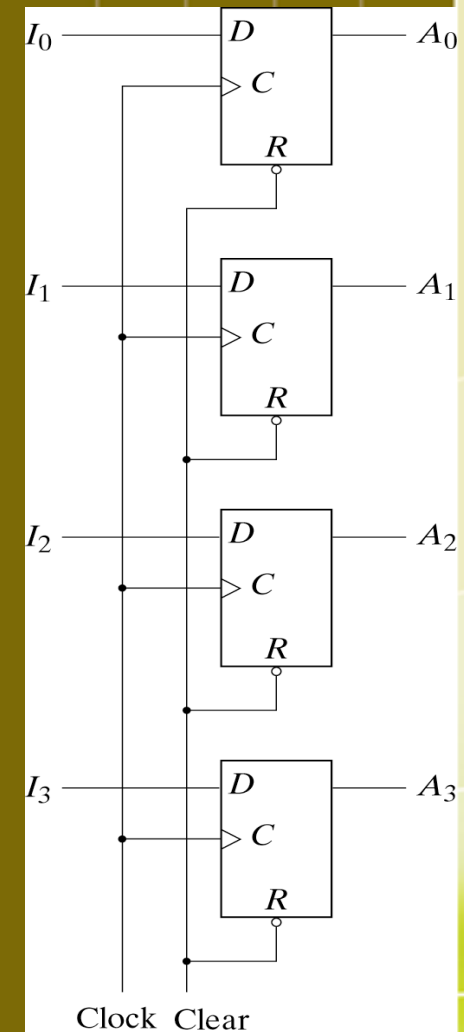


Fig. 6-1 4-Bit Register

# QUESTIONS?

